




Question 4 (10 pts)

In a balanced three-phase load with a positive phase sequence, the complex power is:

$$S = 1500 + j500\sqrt{3} \text{ VA}$$

What are the wattmeter readings?

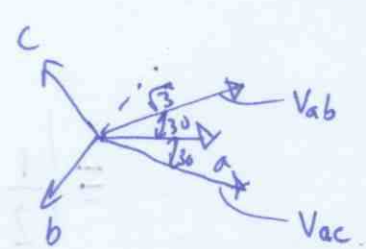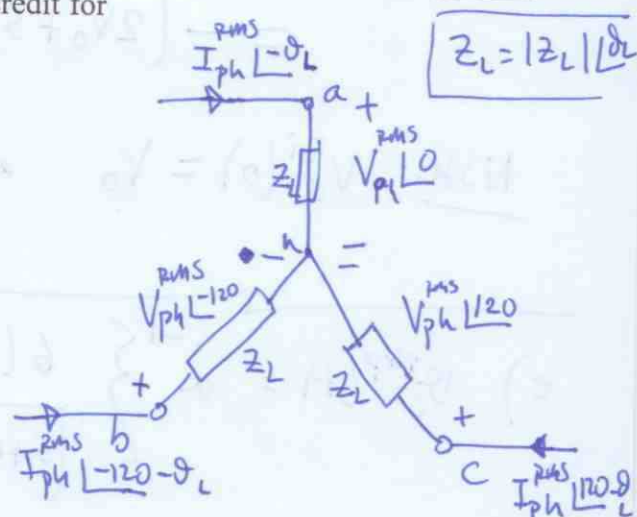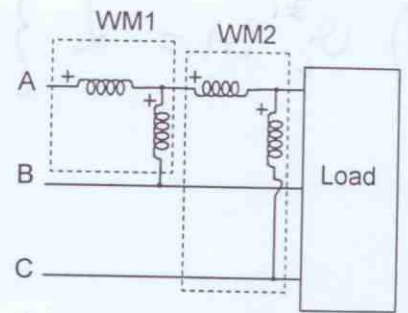NOTE: You have to show your derivations to obtain credit for this question.



$$WM_1 \Rightarrow \text{Re} \{ V_{ab} I_a^* \}$$

$$WM_2 \Rightarrow \text{Re} \{ V_{ac} I_a^* \}$$

$$WM_1 \Rightarrow \text{Re} \left\{ \sqrt{3} V_{ph} \angle 30^\circ I_{ph} \angle +\theta_L \right\}$$

$$= \sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} \cos(30 + \theta_L)$$

$$= \sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} [\cos 30 \cos \theta_L - \sin 30 \sin \theta_L]$$

$$= \sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} \left[\frac{\sqrt{3}}{2} \cos \theta_L - \frac{1}{2} \sin \theta_L \right]$$

$$= \frac{\sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} \cos \theta_L}{2} - \frac{3 V_{ph}^{RMS} I_{ph}^{RMS} \sin \theta_L}{\sqrt{3} \cdot 2}$$

$$= \frac{1500}{2} - \frac{500\sqrt{3}}{\sqrt{3} \cdot 2}$$

$$= 500 \text{ Watt}$$

$$WM_2 \Rightarrow \text{Re} \left\{ \sqrt{3} V_{ph} \angle -30^\circ I_{ph} \angle \theta_L \right\}$$

$$= \sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} \cos(-30 + \theta_L)$$

$$= \frac{1500}{2} + \frac{500\sqrt{3}}{\sqrt{3} \cdot 2} = 1000 \text{ Watt}$$